



Note.1 In real circuit using 150+60 ohm as cross over distortion trim resistor, but this value makes large collector current at Qoutu and Qoutl in simulator.